

EECS251B : Advanced Digital Circuits and Systems

Lecture 14 – Latches

Borivoje Nikolić, Vladimir Stojanović, Sophia Shao



AMD Allies with Ranovus on Data Center Photonics Module
March 6, 2022, EETimes

The co-packaged optical (CPO) demonstration system built by Xilinx and Ranovus. It incorporates the former's Versal ACAP with the latter's Odin Analog-Drive CPO 2.0. (Source: Ranovus)



Recap

- Flip-flop-based (edge-triggered) timing dominates today
- Latch-based timing can increase performance, but needs extra care
- There is also asynchronous design






Design for Performance



Latch Design

Review: MUX

- 2-input MUX

 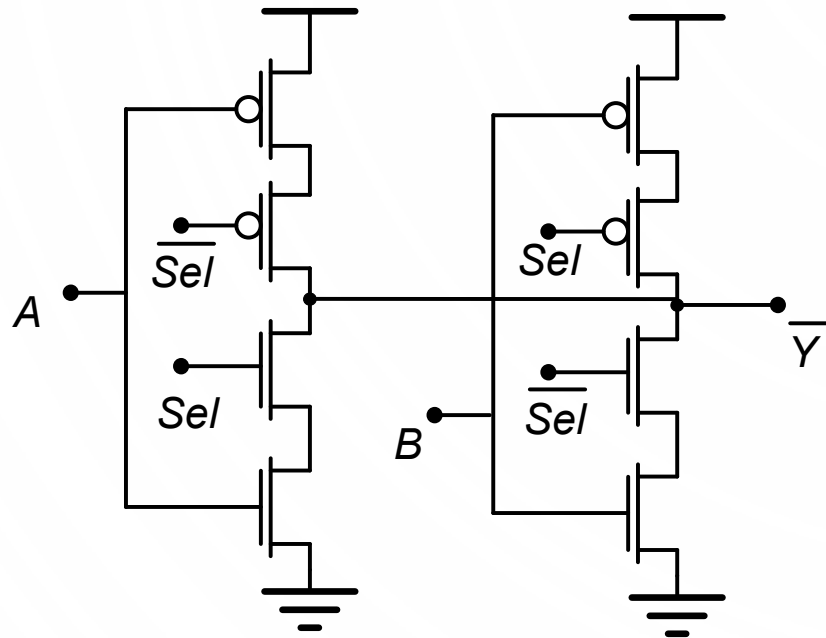 


Review: Transmission Gates

  

LH:




HL:

 





LH:



HL:

 


Review: Transmission Gates

    


Generating Complementary Clocks

- Inverter fork

 


Latch vs. Flip-Flop

 


Latches

Transmission-Gate Latch

 


Usually without contention


C²MOS Latch

 


Latches

 

(a) The transparent high latch (THL)

 

(b) The transparent low latch (TLL)

 

(c) Timing waveforms for the THL

Announcements

- Quiz 1 next Tuesday, in lecture
- Lab 5 due this week
- Midterm reports due next week
 - 4 pages, conference format




Design for Performance

Delay, Setup, Hold


Setup-Hold Time Illustrations

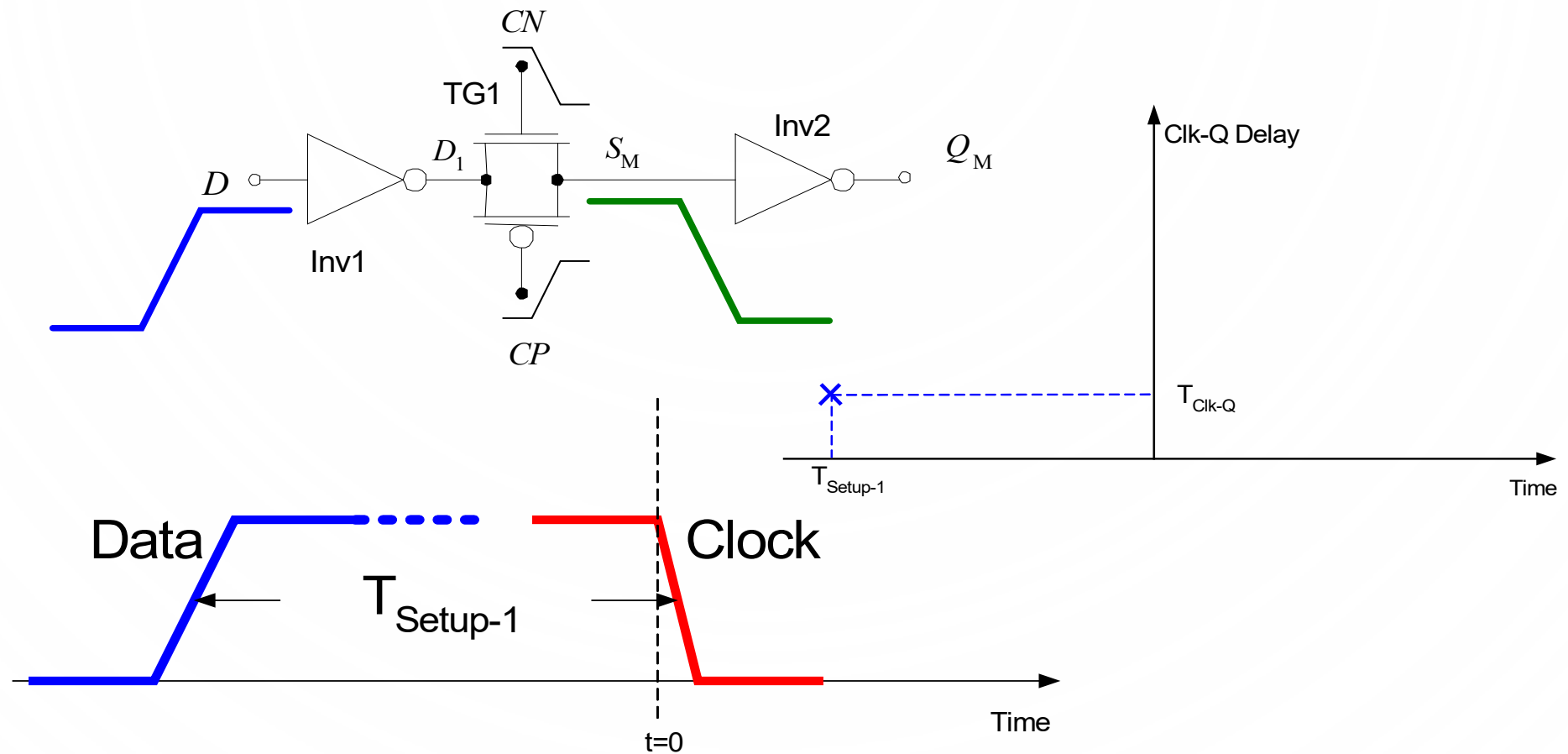Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

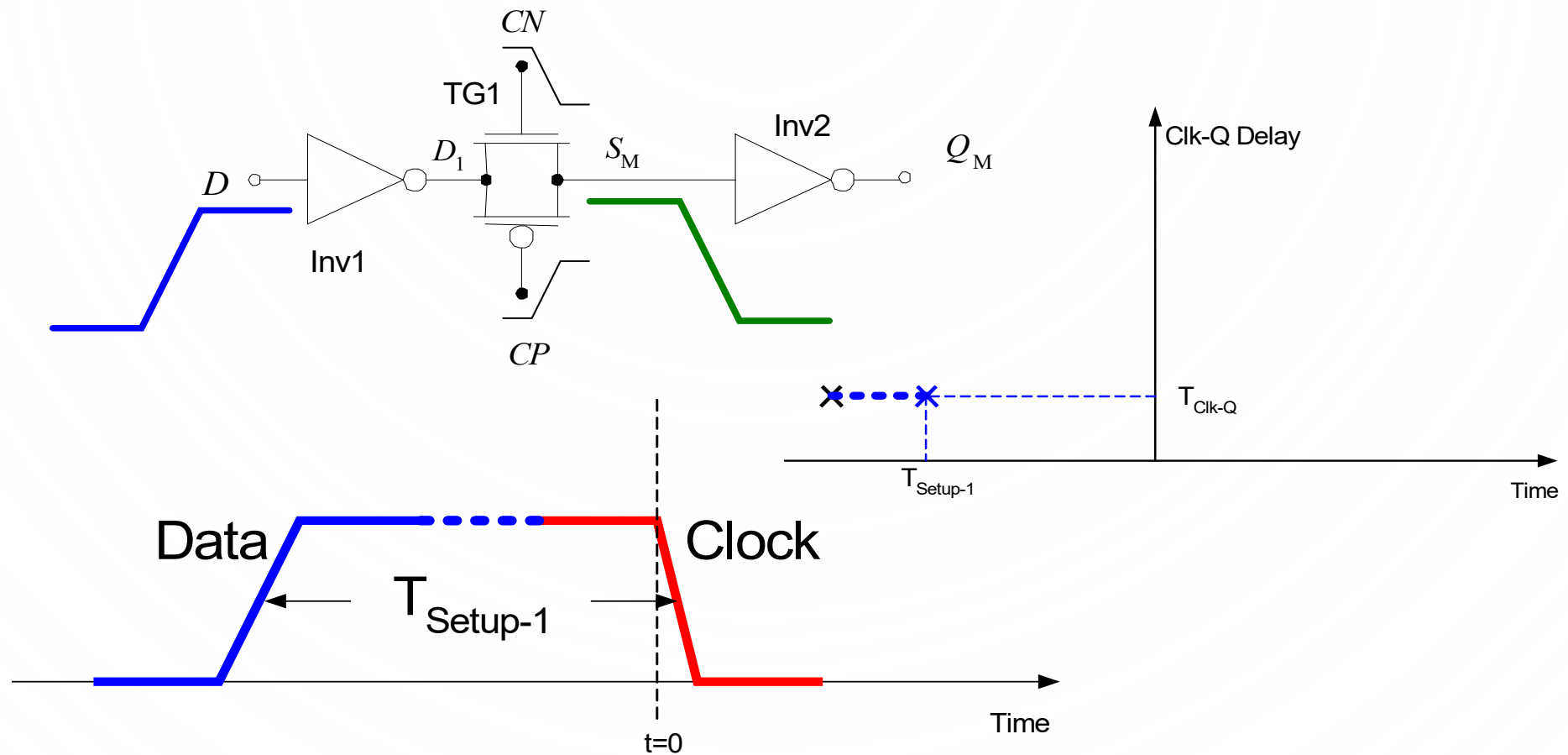Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

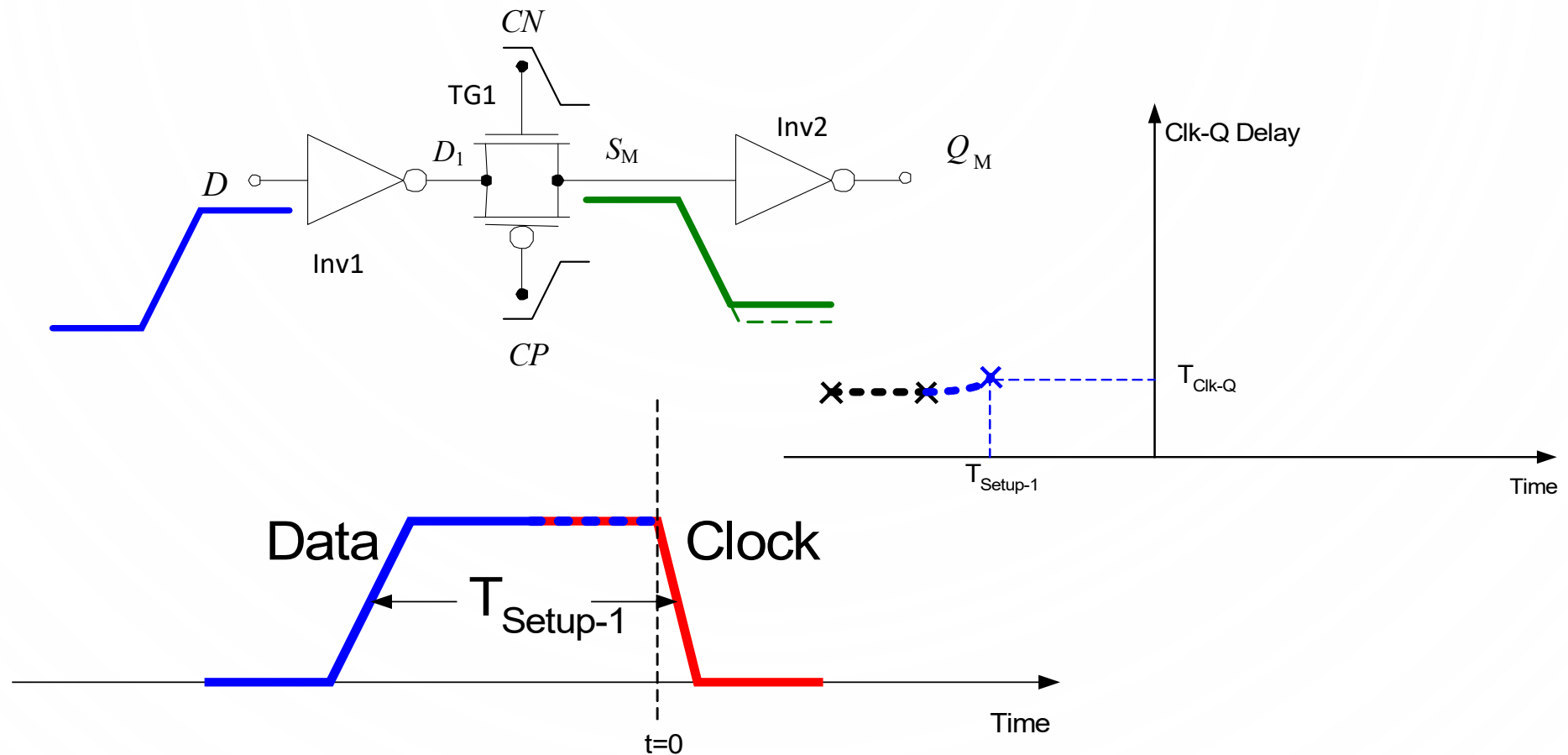Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

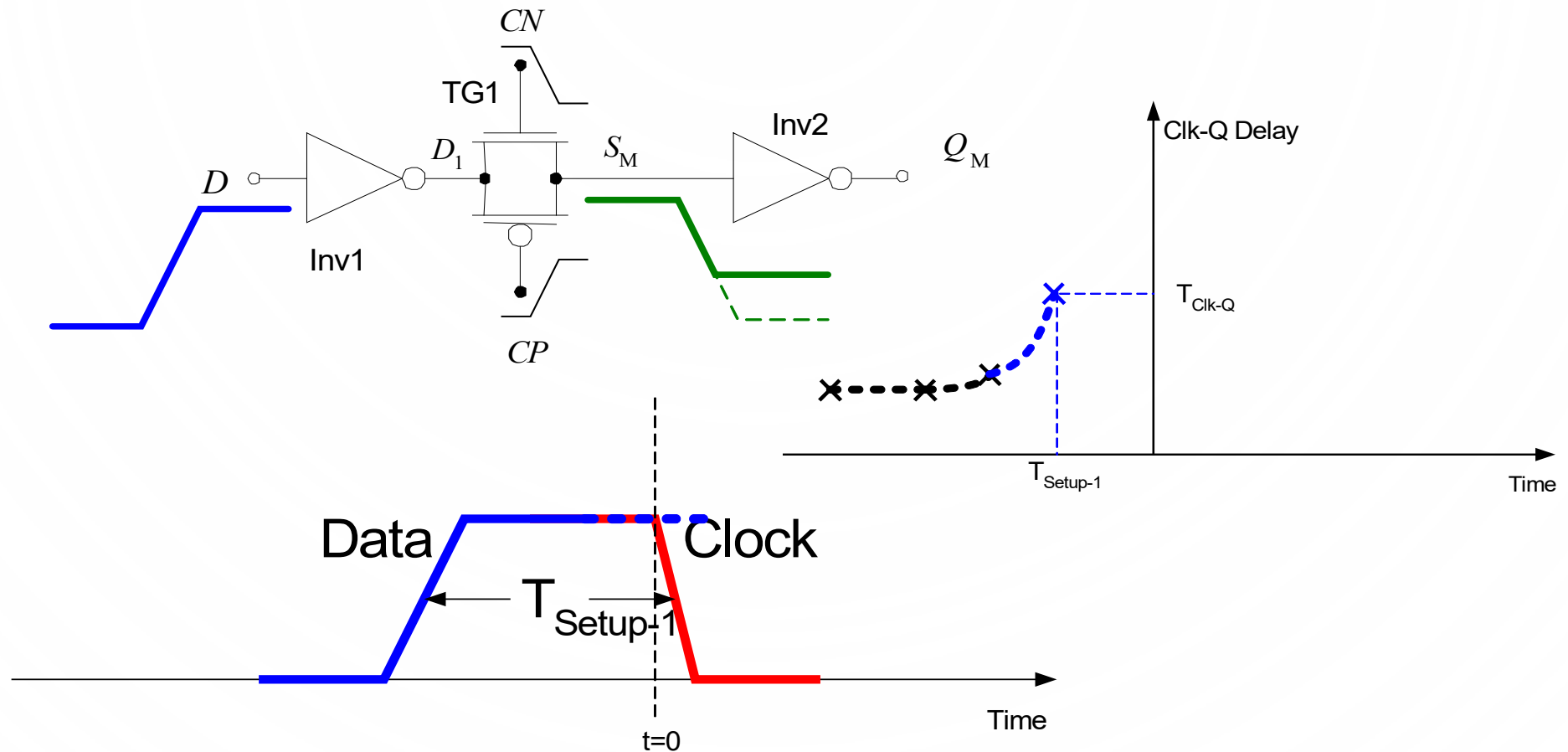Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

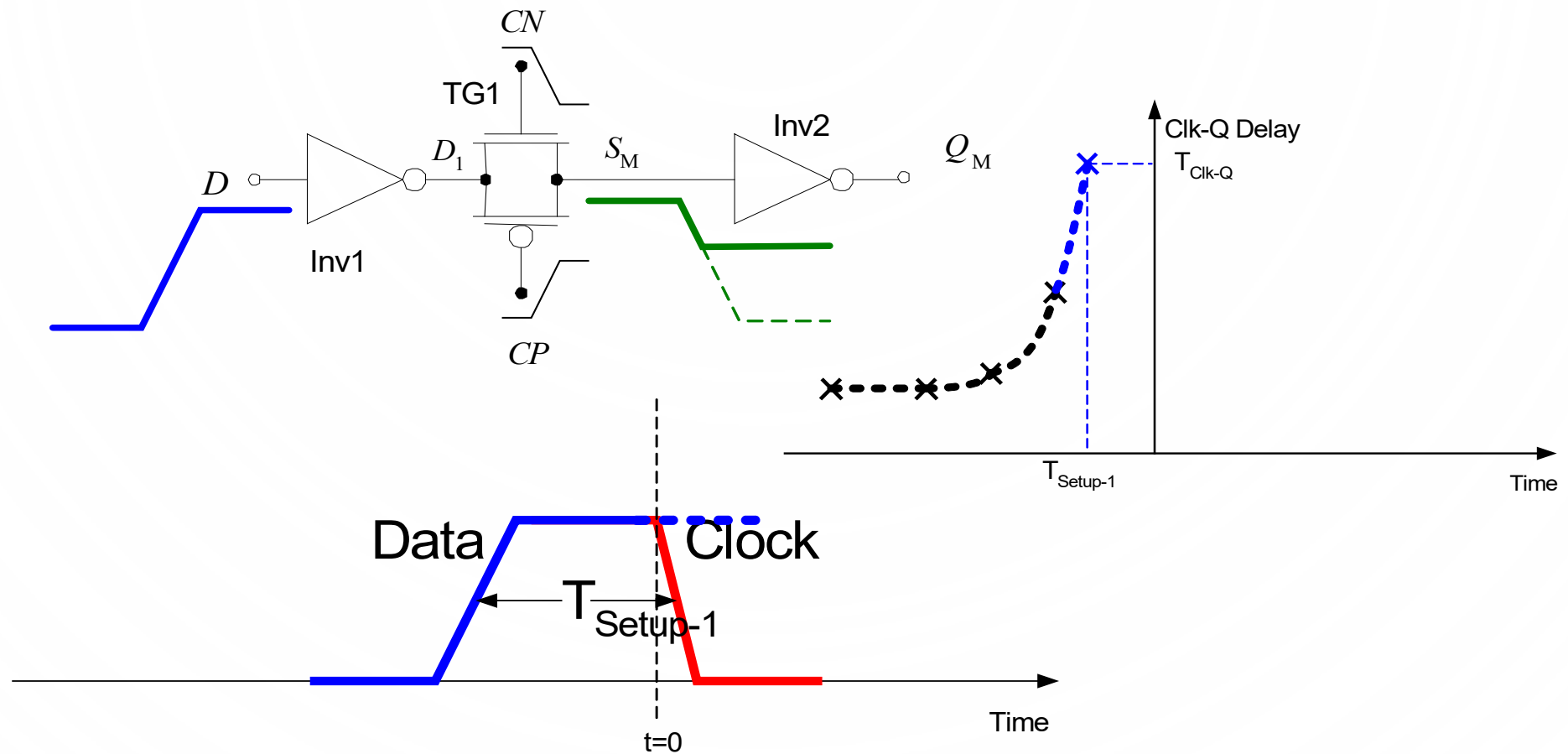Circuit before clock arrival (Setup-1 case)




Setup-Hold Time Illustrations

Hold-1 case

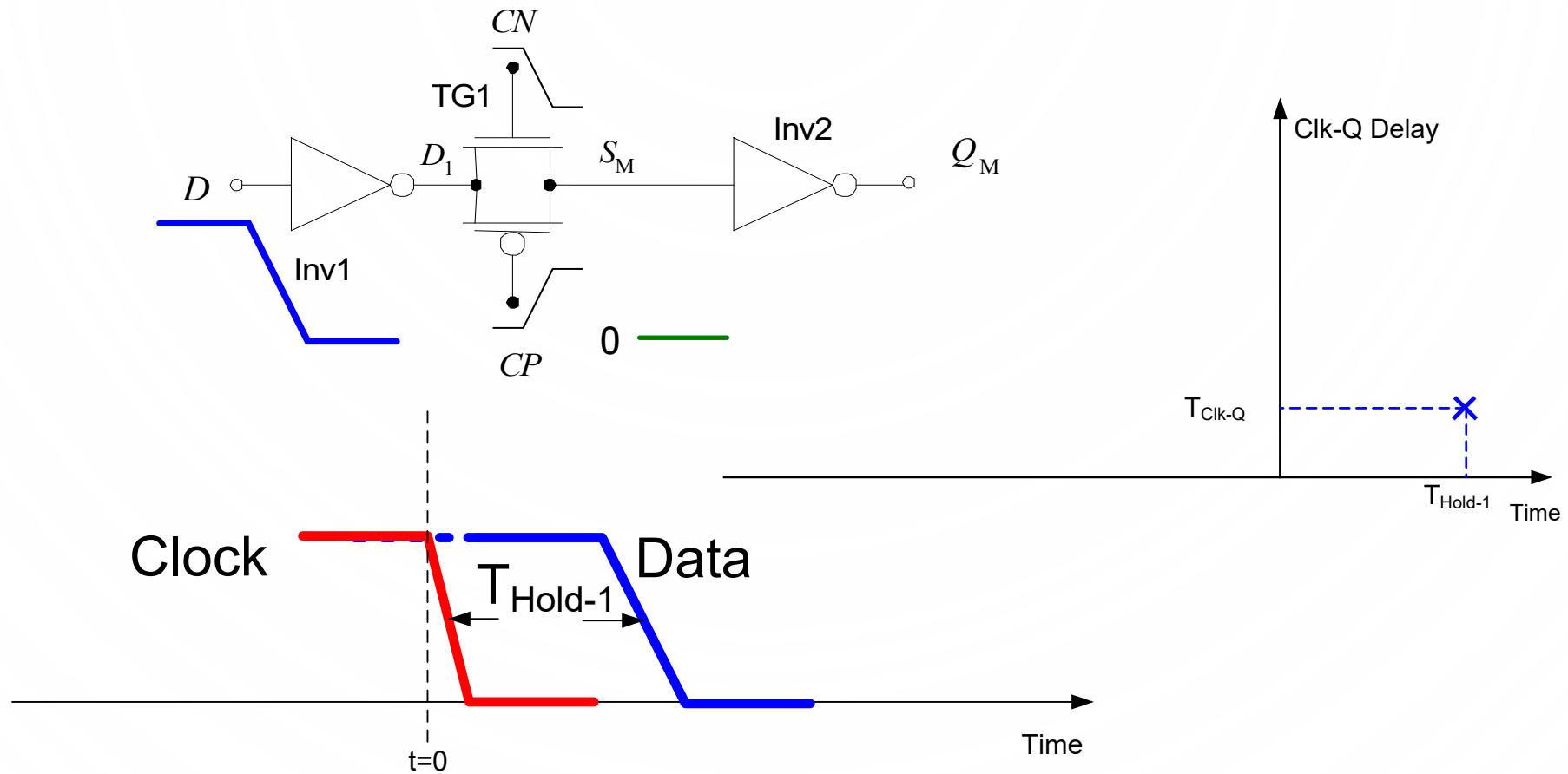


Setup-Hold Time Illustrations

Hold-1 case

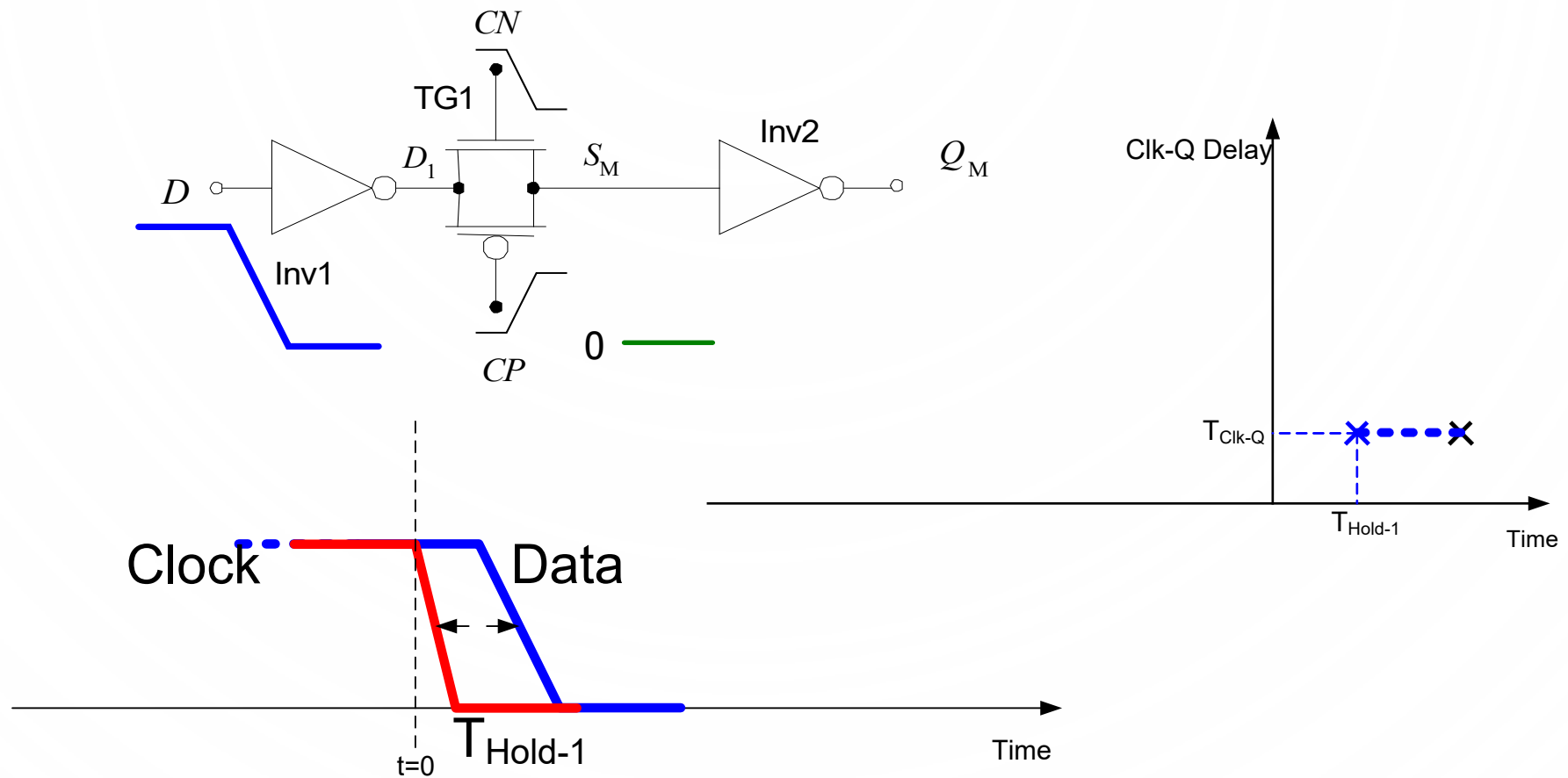


Setup-Hold Time Illustrations

Hold-1 case

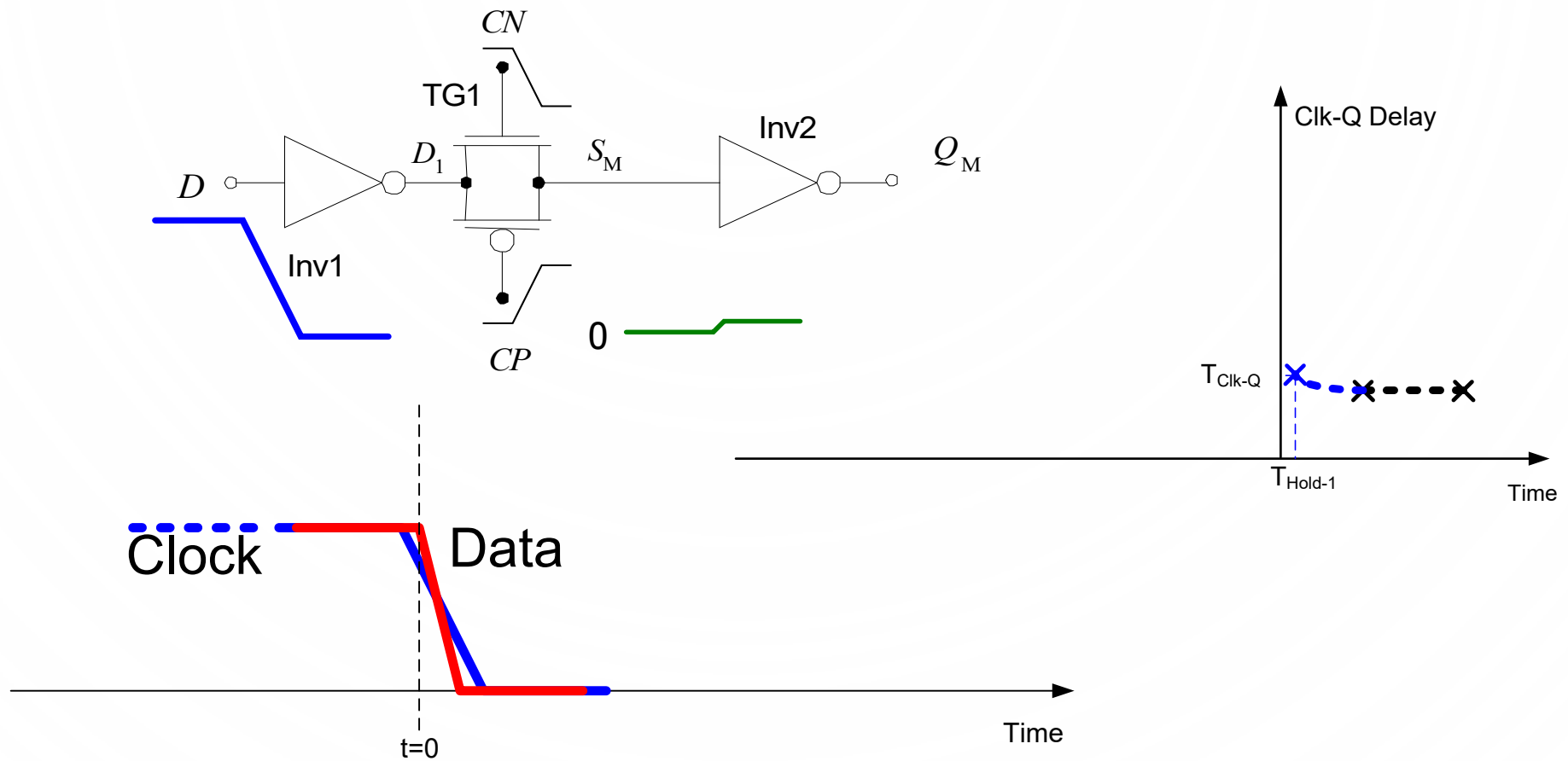


Setup-Hold Time Illustrations

Hold-1 case

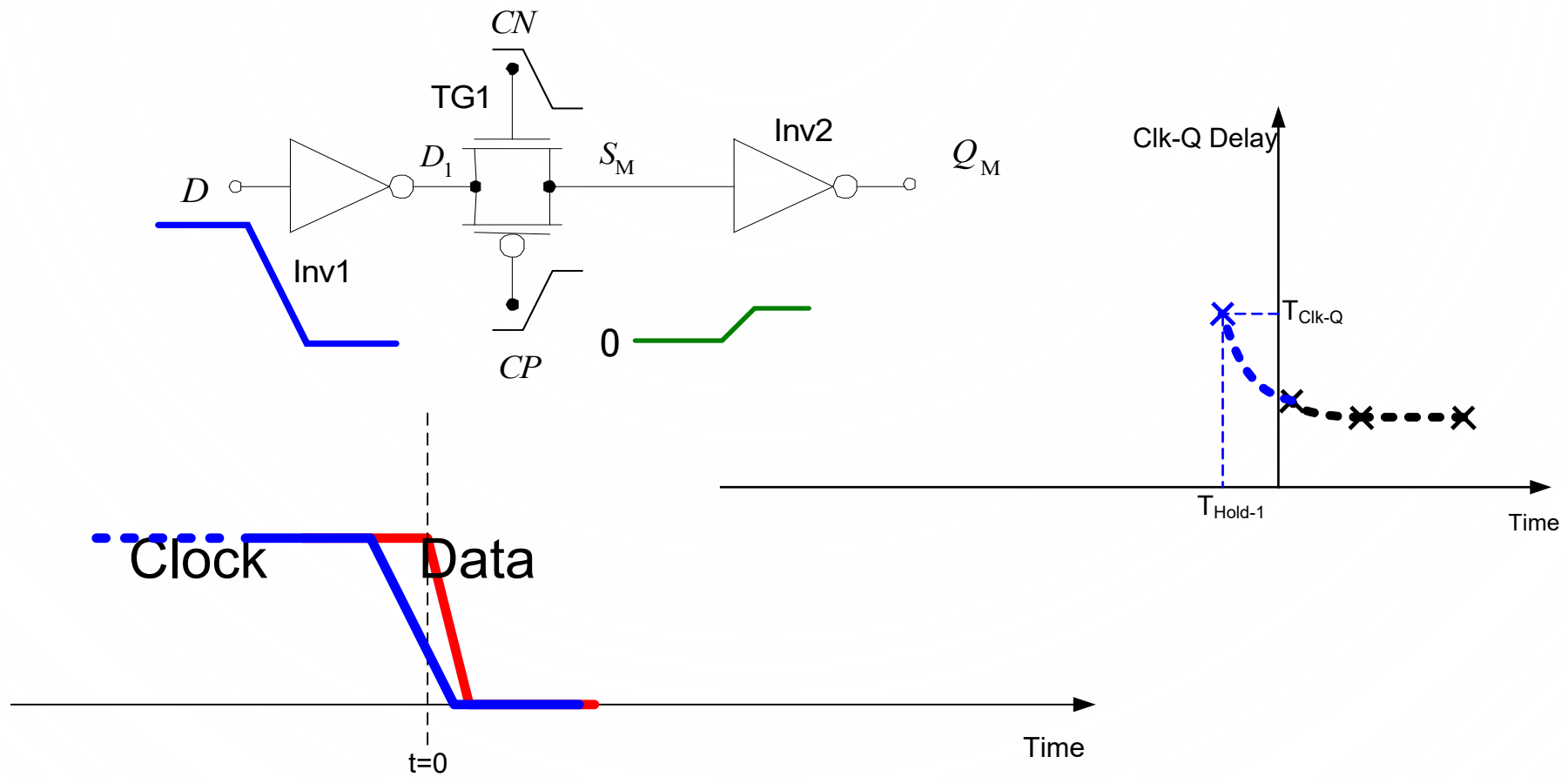


Setup-Hold Time Illustrations


Hold-1 case

 


More Precise Setup Time

 

Latch t_{D-Q} and t_{Clk-Q}

 

t_{setup}

 




Flip-Flops

Key Point

- Two ways to design a flip-flop
 - Latch pair (large majority)
 - Pulsed latch

Latch vs. Flip-Flop

 


Flip-Flops

- Performance metrics
- Delay metrics
 - Insertion delay
 - Inherent race immunity
 - ‘Softness’ (Clock skew absorption)
 - Inclusion of logic
 - Small (+constant) clock load
- Power/Energy Metrics
 - Power/energy
- Design robustness
 - Noise immunity


Scan Test

Types of Flip-Flops


Latch Pair

 

Pulse-Triggered Latch

 

 Flip-Flop (Latch Pair) Clk-Q, setup, hold



Flip-Flop Timing Characterization



- Combinational logic delay is a function of output load and input slope
- Sequential timing (flip-flop):
 - $t_{\text{clk-q}}$ is function of output load and clock rise time
 - t_{Su} , t_{H} are functions of D and Clk rise/fall times

Pulse-Triggered Latches

- First stage is a pulse generator
 - generates a pulse (glitch) on a rising edge of the clock
- Second stage is a latch
 - captures the pulse generated in the first stage
- Pulse generation results in a negative setup time
- Frequently exhibit a soft edge property
- Note: power is always consumed in the pulse generator
 - Often shared by a group (register)


Pulsed Latch

Simple pulsed latch

  

Kozu, ISSCC'96


Intel/HP Itanium 2

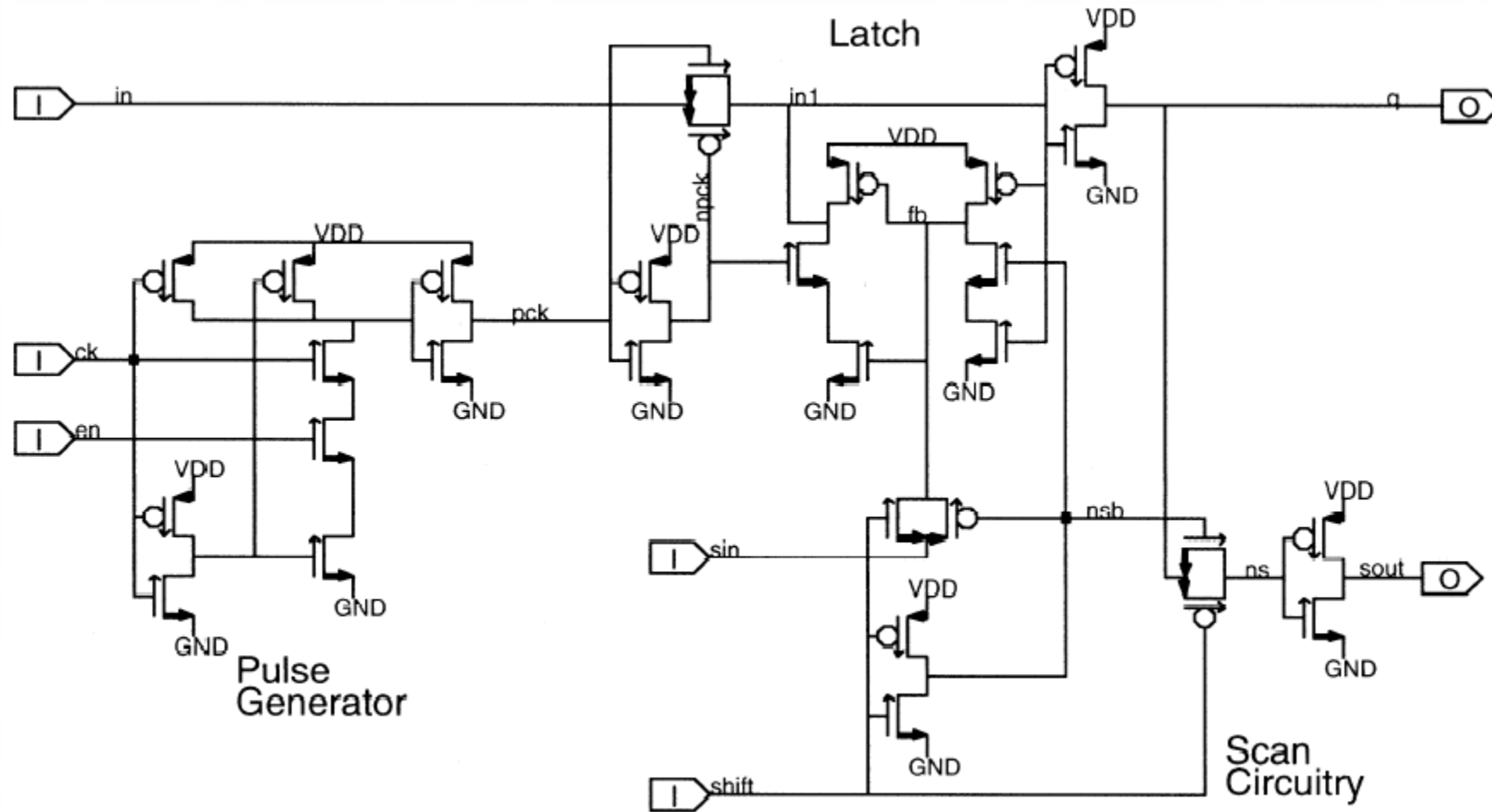

Naffziger, ISSCC'02


Pulsed Latches

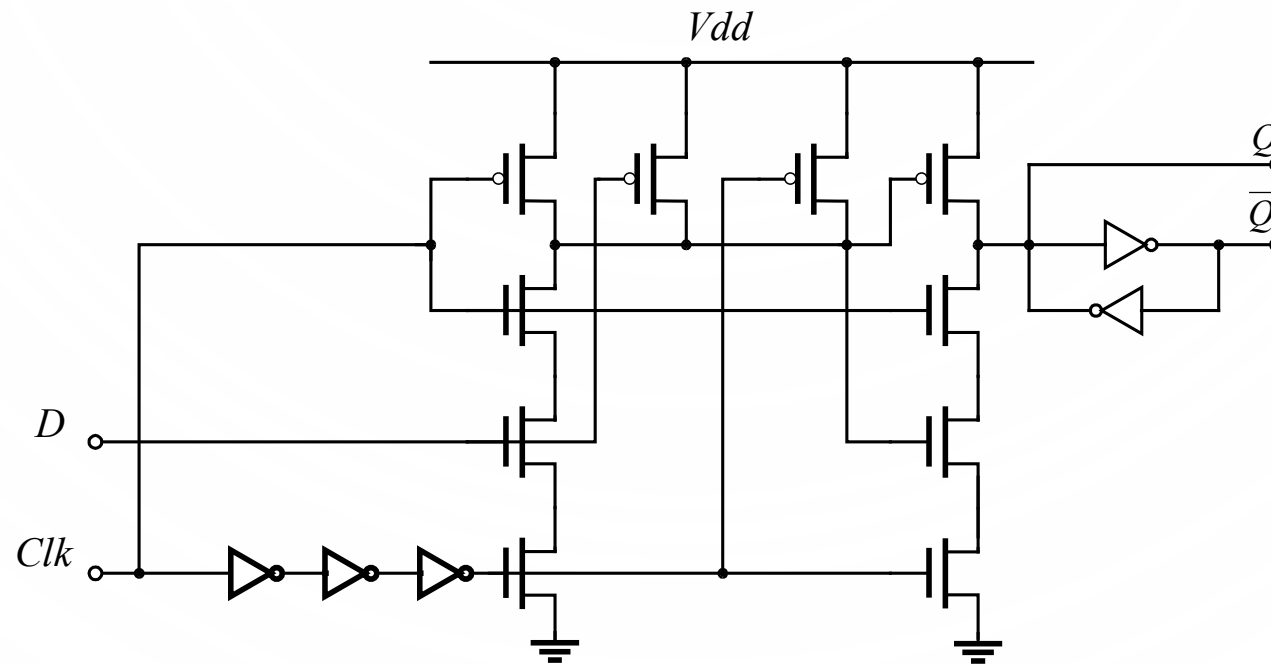Hybrid Latch Flip-Flop, AMD K-6
Partovi, ISSCC'96



HLFF Operation

 1-0 and 0-1 transitions at the input with 0ps setup time




VDD=2.3v, 85°C, Typical Devices
 $C_{clk} = 60\text{ff}$, $C_{qb} = 300\text{ff}$

$T_{cq} = T_{dq} = 340\text{ps}$
 $T_{hold} = 180\text{ps}$
 $T_{su(min)} = -90\text{ps}$

Hybrid Latch Flip-Flop


Skew absorption

 

Partovi et al, ISSCC'96

Pulsed Latches

7474, from mid-1960's

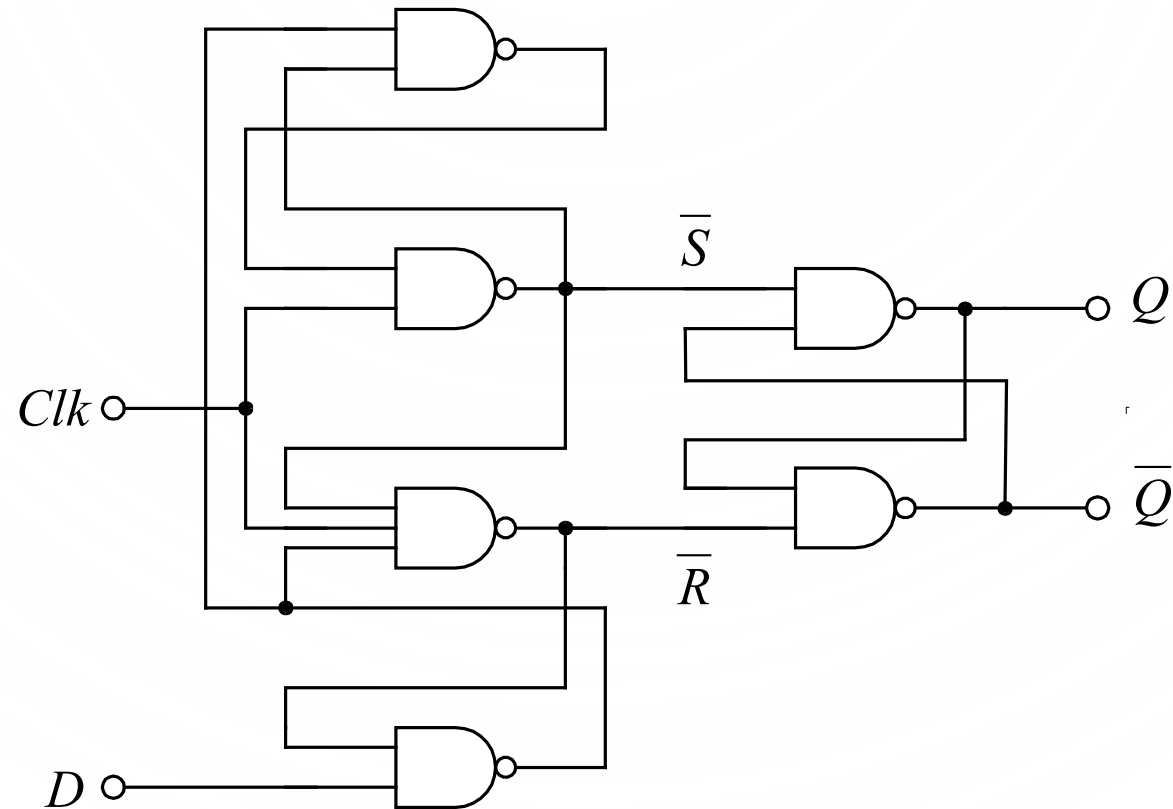

Pulsed Latches

Sense-amplifier-based flip-flop, Matsui 1992.
DEC Alpha 21264, StrongARM 110

First stage is a sense amplifier, precharged to high, when $Clk = 0$


After rising edge of the clock sense amplifier generates the pulse on

S or R


The pulse is captured in

S-R latch

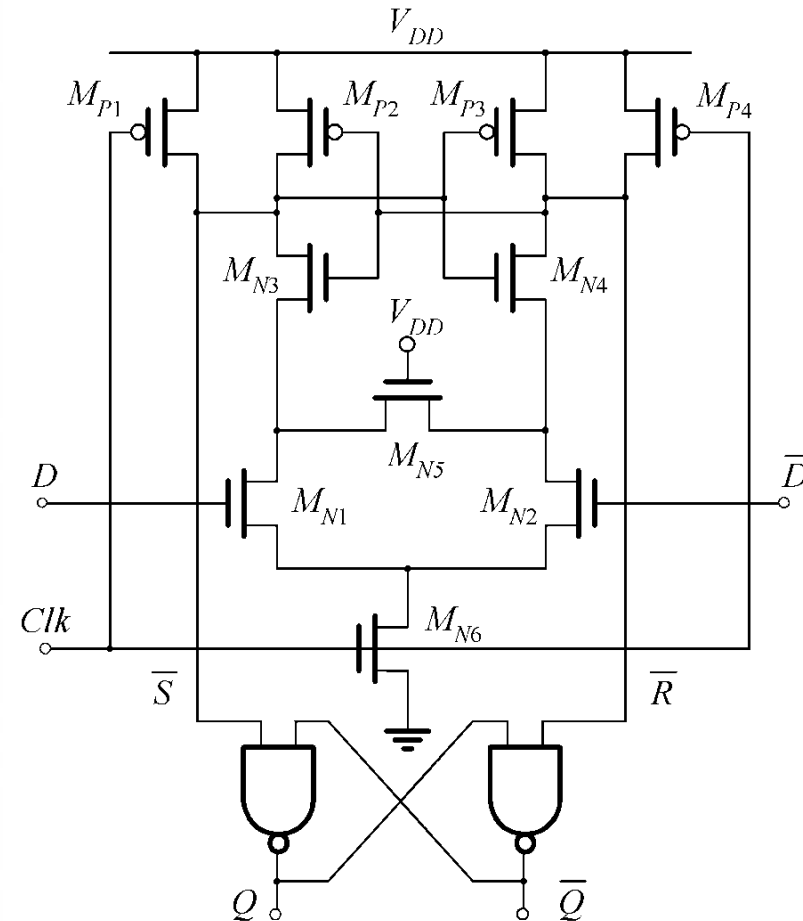Cross-coupled NAND has different propagation delays of rising and falling edges




Sense Amplifier-Based Flip-Flop

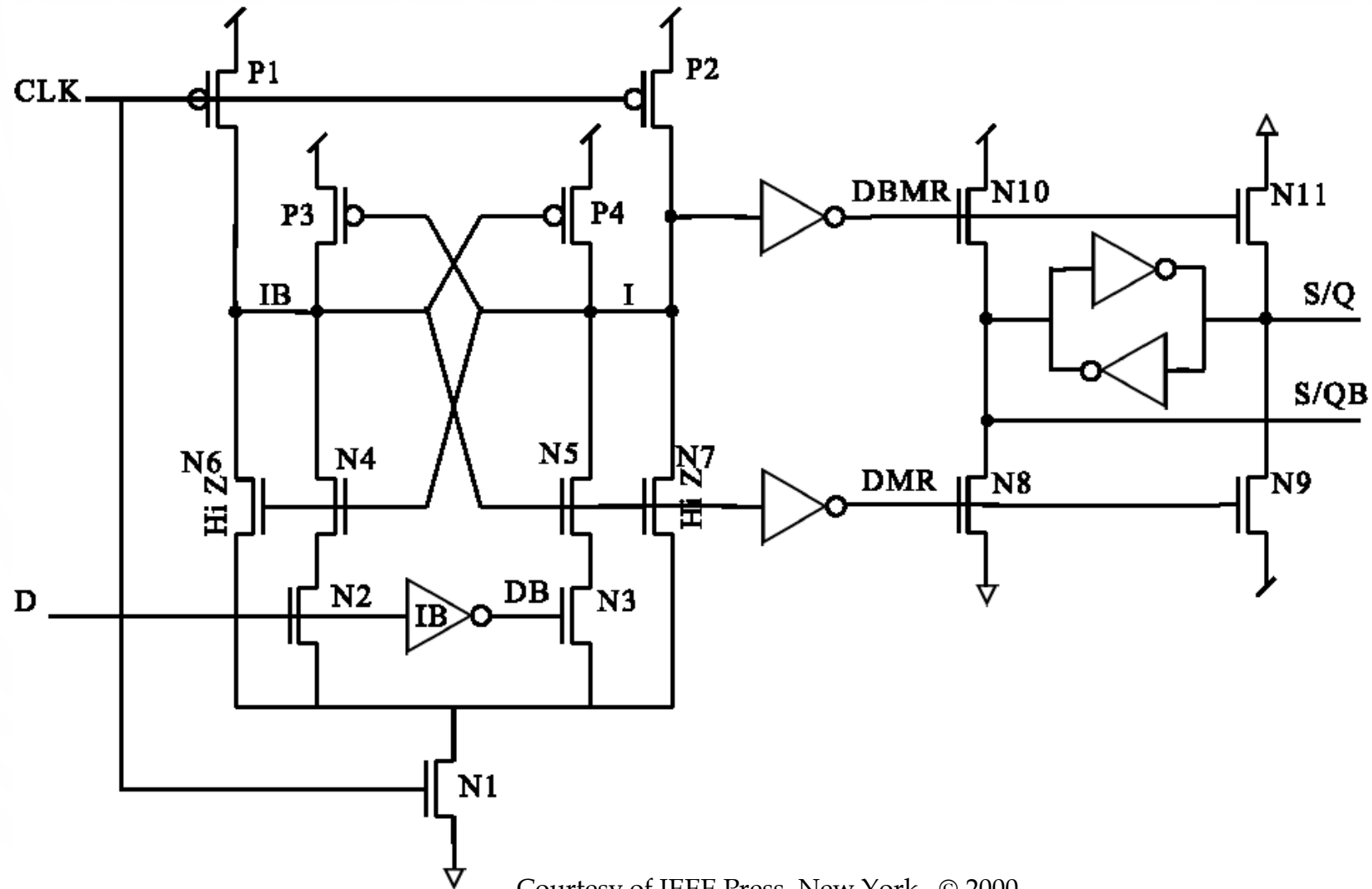

Courtesy of IEEE Press, New York. © 2000

Sampling Window Comparison

 

Naffziger, JSSC 11/02

Summary

- Logical effort can be used to analyze latch timing
 - Clk-Q, setup, hold
- Flip-flops:
 - Latch pairs
 - Pulse triggered

Next Lecture

- Variability