

# EECS251B : Advanced Digital Circuits and Systems

## Lecture 20 – Low Power Design

Borivoje Nikolić, Vladimir Stojanović, Sophia Shao



IEEE MICRO, Nov/Dec 2021  
Microprocessor at 50: Looking Back and Looking Forward  
Special issue on 50 years of a microprocessor



Advertisement in the Electronics News Weekly in November 1971 announcing the Intel 4004.



EECS251B L20 LOW-POWER DESIGN



### Recap

- Power is a primary design constraint
  - In both cloud and edge systems
- Excess performance traded off for power savings

### Optimal Processors

- Processors used to be optimized for performance
  - Optimal logic depth was found to be 8-11 FO4 delays in superscalar processors
  - 1.8-3 FO4 in sequentials, rest in combinatorial
    - Kunkel, Smith, ISCA'86
    - Hrskesh, Jouppi, Farkas, Burger, Keckler, Shivakumar, ISCA'02
    - Harstein, Puzak, ISCA'02
    - Sprangle, Carmean, ISCA'02
- But those designs have very high power dissipation
  - Need to optimize for both performance and power/energy

### Architectural Optimizations



### From System View: What is the Optimum?

- How do sensitivities relate to more traditional metrics:
  - Power per operation (MIPS/W, GOPS/W, TOPS/W)
  - Energy per operation (Joules per op)
  - Energy-delay product
- Can be reformatted as a goal of optimizing power x delay<sup>n</sup>
  - n = 0 – minimize power per operation
  - n = 1 – minimize energy per operation
  - n = 2 – minimize energy-delay product
  - n = 3 – minimize energy-(delay)<sup>2</sup> product

### Optimization Problem

- Set up optimization problem:
  - Maximize performance under energy constraints
  - Minimize energy under performance constraints
- Or minimize a composite function of E<sup>n</sup>D<sup>m</sup>
  - What are the right n and m?
- n = 1, m = 1 is EDP – improves at lower V<sub>DD</sub>
- n = 1, m = 2 is invariant to V<sub>DD</sub>
  - E ~ CV<sub>DD</sub><sup>2</sup>
  - D ~ 1/V<sub>DD</sub>


### Hardware Intensity

- Introduced by Zyuban and Strenski in 2002.
- Measures where is the design on the Energy-Delay curve
- Parameter in cost function optimization


$$F_c = (E/E_0)(D/D_0)^\eta \quad 0 \leq \eta < +\infty,$$

$$\eta = - \frac{D \partial E}{E \partial D} \bigg|_V$$

 Slope of the optimal E-D curve at the chosen design point



### Optimum Across Hierarchy Layers

 


Optimal logic depth in pipelined processors is ~18FO4  
Relatively flat in the 16-22FO4 range

Zyuban et al, TComp'04

## Architectural Tradeoffs


- H, Mair, ISSCC'20

 

EECS251B L20 LOW-POWER DESIGN
 
## Architectural Tradeoffs: Tri-Gear

- HP: High performance (ARM Cortex A78, optimized for speed, 3.0GHz)
- BP: Balanced performance (ARM Cortex A78, optimized for power, 2.6GHz)
- HE: High efficiency (ARM A55, 2.0GHz)



## Announcements


- Quiz 2 today
- Homework 3 due next week

EECS251B L20 LOW-POWER DESIGN

## Circuit-Level Tradeoffs



## Alpha-Power Based Delay Model

 

$$t_{pi} = \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left( 1 + \frac{C_{L,i}}{C_{in,i}} \right)$$

$$D = \sum t_{pi} = \sum \frac{K_d V_{DD}}{(V_{DD} - V_{Th})^\alpha} \left( 1 + \frac{W_{L,i}}{W_{in,i}} \right)$$

EECS251B L20 LOW-POWER DESIGN

## Energy Models

### Switching

$$E_{Sw} = \alpha_{0 \rightarrow 1} (C_{L,i} + C_{int,i}) V_{DD}^2$$



### Leakage


$$E_{Lk} = W_{in,i} I_0 e^{\frac{-(V_{Th} - \gamma V_{DD})}{n V_T}} V_{DD} D$$

## Sizing, Supply, Threshold Optimization

- Transistor sizing can yield large power savings with small delay penalties
  - Gate sizing
  - Beta-ratio adjustments  $\beta = Wp/Wn$
  - (Stack resizing)
- Supply voltage affects both active and leakage energy
- Threshold voltage affects primarily the leakage

EECS251B L20 LOW-POWER DESIGN

## Apply to Sizing of an Inverter Chain

 

Unconstrained energy: find  $\min D = \sum t_{pi}$

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}} \quad W_j = \sqrt{W_{j-1} W_{j+1}}$$

Constrained energy: find  $\min D$ , under  $E < E_{max}$   
Where  $E = \sum e_i$

EECS251B L20 LOW-POWER DESIGN

## Constrained Optimization

- Find  $\min(D)$  subject to  $E = E_{\max}$ 
  - Constrained function minimization
- E.g. Lagrange multipliers

$$\Lambda(x) = D(x) + \lambda(E(x) - E_{\max})$$

$$\frac{\partial \Lambda}{\partial x} = 0$$


- Can solve analytically for  $x = W_i, V_{DD}, V_{Th}$

Or dual:

$$K(x) = E(x) + \lambda(D - D_{\max})$$

## Inverter Chain: Sizing Optimization

## Inverter Chain: Sizing Optimization

 

$$W_j = \sqrt{\frac{W_{j-1}W_{j+1}}{1 + \lambda W_{j-1}}}$$

[Ma, Franzon, IEEE JSSC, 9/94]

$$\lambda = -\frac{2KV_{DD}^2}{\tau_{nom}S_W}$$

$$S_W \propto \frac{e_j}{f_j - f_{j-1}}$$

$e_j$  - energy per stage  
 $f_j$  - fanout per stage

Stojanovic, ICCAD'02

- Variable taper achieves minimum energy
- Reduce number of stages at large  $d_{inc}$

## Sensitivity to Sizing and Supply

- Gate sizing ( $W_i$ )


$$-\frac{\partial E_{sw}}{\partial D} \frac{\partial W_j}{\partial W_j} = \frac{e_j}{\tau_{nom}(f_j - f_{j-1})}$$

$\infty$  for equal  $f_{eff}$   
( $D_{min}$ )

- Supply voltage ( $V_{dd}$ )

$$-\frac{\partial E_{sw}}{\partial D} \frac{\partial V_{DD}}{\partial V_{DD}} = \frac{E_{sw}}{D} 2 \frac{1 - x_v}{\alpha - 1 + x_v}$$
 
$$x_v = (V_{th} + \Delta V_{th}) / V_{dd}$$




## Sensitivity to $V_{th}$

- Threshold voltage ( $V_{th}$ )


$$-\frac{\partial E}{\partial D} \frac{\partial \Delta V_{th}}{\partial \Delta V_{th}} = P_{Lk} \left( \frac{V_{DD} - V_{th} - \Delta V_{th}}{\alpha n V_t} - 1 \right)$$

 Low initial leakage  
 $\Rightarrow$  speedup comes for "free"



## Scaling Supplies

## Reducing $V_{dd}$

 

$$P \times t_d = E_t = C_L \cdot V_{dd}^2$$


$$\frac{E(V_{dd}=2)}{E(V_{dd}=5)} = \left( \frac{C_L}{C_L} \right) \cdot \left( \frac{2}{5} \right)^2$$

$$E(V_{dd}=2) = 0.16 E(V_{dd}=5)$$

- Strong function of voltage ( $V^2$  dependence).
- Relatively independent of logic function and style.
- Power Delay Product Improves with lowering  $V_{DD}$ .

Chandrakasan, JSSC'92

## Lower $V_{DD}$ Increases Delay

 


$$T_d = \frac{C_L \cdot V_{dd}}{I}$$

$$I \sim (V_{dd} - V_t)^2$$


$$\frac{T_d(V_{dd}=2)}{T_d(V_{dd}=5)} = \frac{(2)^2 \cdot (5 - 0.7)^2}{(5)^2 \cdot (2 - 0.7)^2} \approx 4$$

- Relatively independent of logic function and style.

## Trade-off Between Power and Delay

 

 
## Architecture Trade-off for Fixed-rate Processing Reference Datapath




- Critical path delay  $\Rightarrow T_{\text{adder}} + T_{\text{comparator}} (= 25\text{ns})$   
 $\Rightarrow f_{\text{ref}} = 40\text{Mhz}$
- Total capacitance being switched =  $C_{\text{ref}}$
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath =  $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$   
from [Chandrakasan92] (IEEE JSSC)

## Parallel Datapath

 

- The clock rate can be reduced by half with the same throughput  $\Rightarrow f_{\text{par}} = f_{\text{ref}} / 2$
- $V_{\text{par}} = V_{\text{ref}} / 1.7$ ,  $C_{\text{par}} = 2.15C_{\text{ref}}$
- $P_{\text{par}} = (2.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 (f_{\text{ref}}/2) = 0.36 P_{\text{ref}}$

## Pipelined Datapath

 

- Critical path delay is less  $\Rightarrow \max [T_{\text{adder}}, T_{\text{comparator}}]$
- Keeping clock rate constant:  $f_{\text{pipe}} = f_{\text{ref}}$   
 Voltage can be dropped  $\Rightarrow V_{\text{pipe}} = V_{\text{ref}} / 1.7$
- Capacitance slightly higher:  $C_{\text{pipe}} = 1.15C_{\text{ref}}$
- $P_{\text{pipe}} = (1.15C_{\text{ref}}) (V_{\text{ref}}/1.7)^2 f_{\text{ref}} = 0.39 P_{\text{ref}}$

## A Simple Datapath: Summary

Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	1
Pipelined datapath	2.9V	1.3	0.39
Parallel datapath	2.9V	3.4	0.36
Pipeline-Parallel	2.0V	3.7	0.2

## Multiple Supplies




## Multiple Supply Voltages

- Block-level supply assignment ("power domains" or "voltage islands")
  - Higher throughput/lower latency functions are implemented in higher  $V_{DD}$
  - Slower functions are implemented with lower  $V_{DD}$
  - Often called "Voltage islands"
  - Separate supply grids, level conversion performed at block boundaries
- Multiple supplies inside a block
  - Non-critical paths moved to lower supply voltage
  - Level conversion within the block
  - Physical design challenging
  - (Not used in practice)

## Power Domains
 
## Practical Examples


- Intel Skylake (ISSCC'16)
  - Four power planes indicated by colors



SA Power planes

## Practical Examples

- Intel 28-core Skylake-SP (ISSCC'18)


 


- Vcc: core supply (per core)
- Vccclm: Un-core supply
- Vccsa: System Agent supply
- Vccio: Infrastructure supply
- Vccsfr: PLL supply
- Vccddr: DDR logic supply
- Vccddra: DDR I/O supply

- 9 primary VCC domains are partitioned into 35 VCC planes

  
## Leakage Issue

- Driving from  $V_{DDL}$  to  $V_{DDH}$ 
  - Level converter



 
## Multiple Supplies Within A Block

- Downsizing, lowering the supply on the critical path will lower the operating frequency
- Downsize (lowering supply) non-critical paths
  - Narrows down the path delay distribution
  - Increases impact of variations




## Multiple Supplies in a Block

### Conventional Design

 

### CVS Structure

 


Lower  $V_{DD}$  portion is shaded  
"Clustered voltage scaling"

M. Takahashi, ISSCC'98.


## Multiple Supplies in a Block

### CVS

 


Usami'98

### Layout:

 


## Level-Converting Flip-Flop

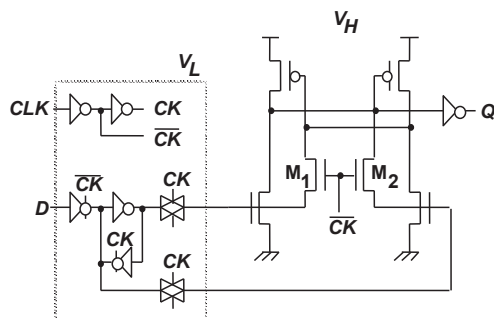
 
## Summary

- Power-performance tradeoffs
  - Sizing
  - Supplies
  - Thresholds
- Lowering supplies
- Multiple supply voltages



## Next Lecture

- Low-power design
  - Dynamic voltage-frequency scaling
  - Clock gating

